

Student reg.no: 19BCE0298

Student Name: Dhanush Kumaar J

Course Code: CSE1003

Course Name: Digital Logic and Design

Due Date: 28-10-2021

Date of Submission: 28-10-2021


Slot & Semester: L5+L6 FALL-2021-2022

Faculty: Dr. N.Sangeetha

1. Construct the circuits of the below code converters using LT spice

BCD to Excess 3

Simulation Circuit

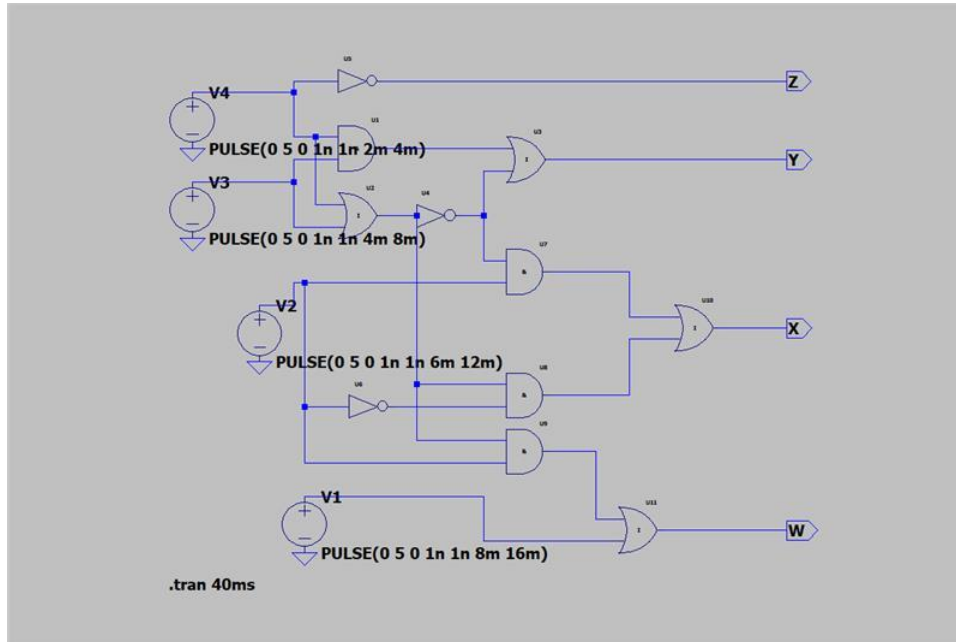


Output waveform




Binary to gray

Simulation Circuit

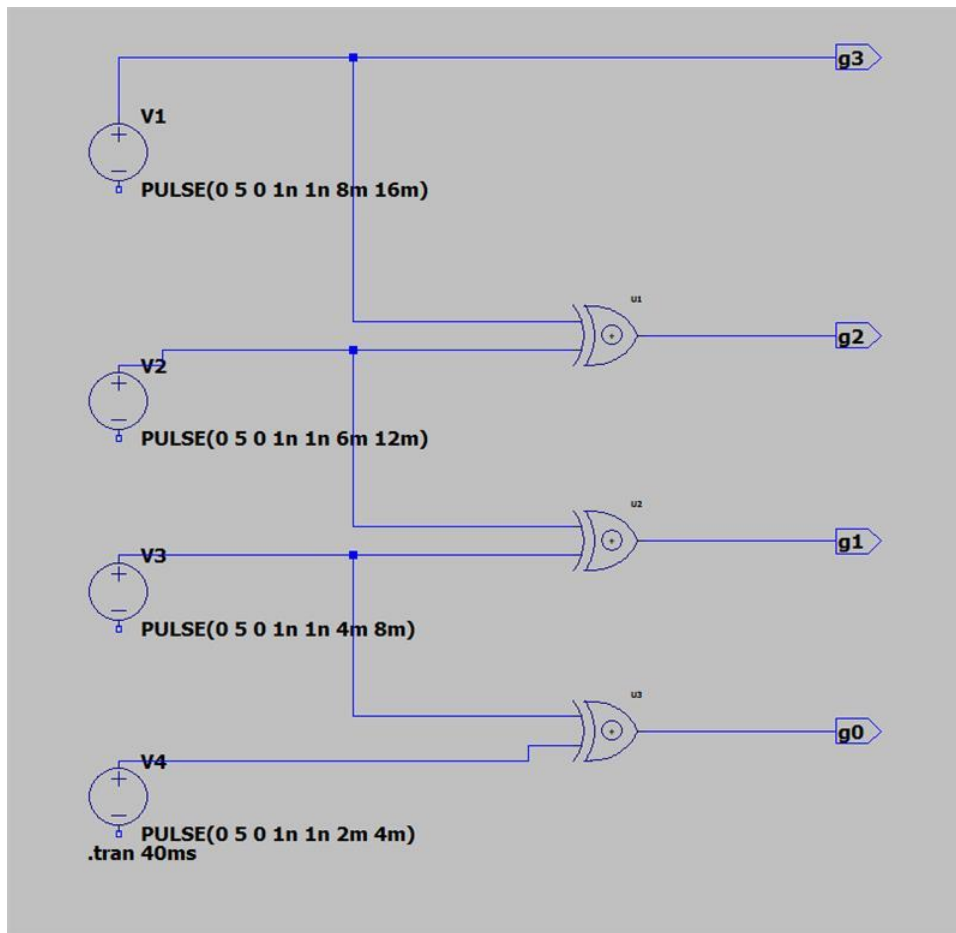


Output waveform

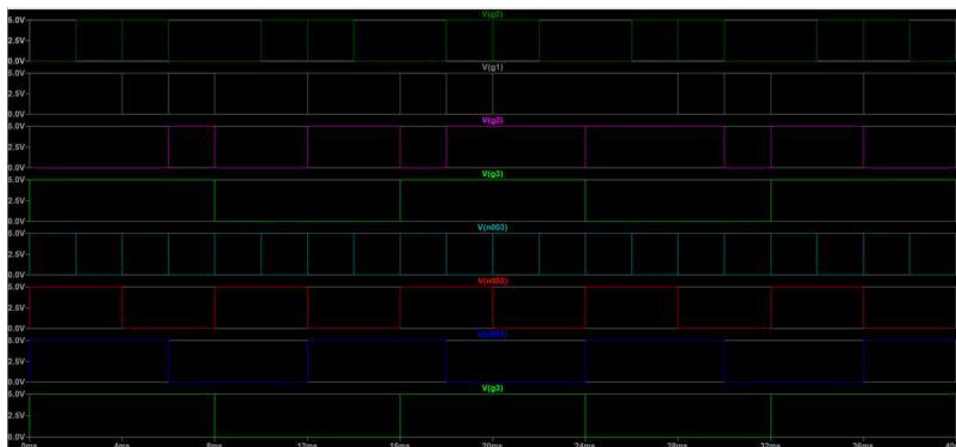


Gray to Binary

Simulation Circuit

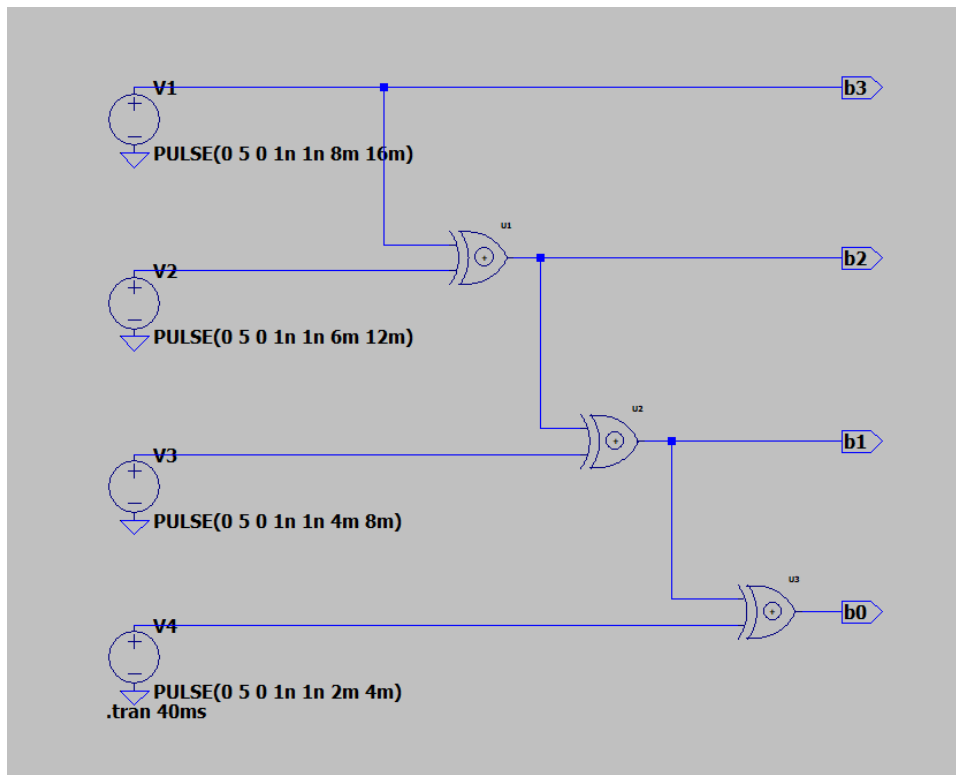


Output waveform

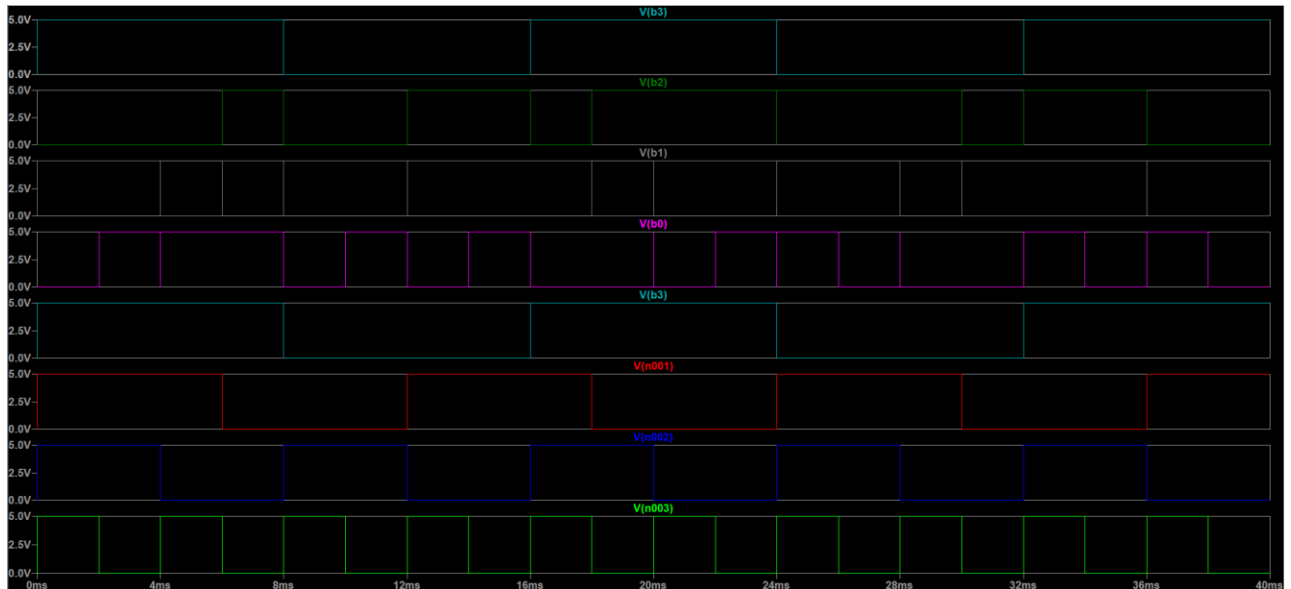

2. Construct 4 bit binary parallel adder using LT spice

Simulation Circuit

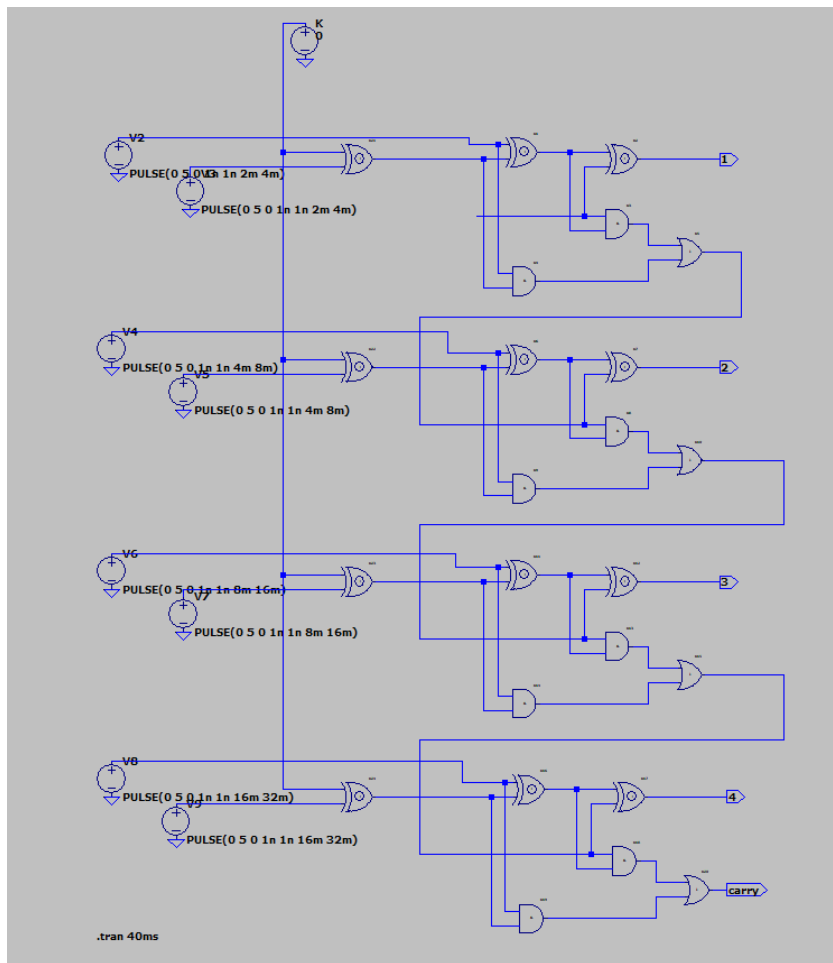

Output waveform

